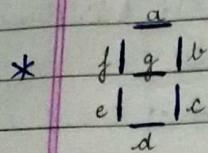


BCD to seven segment code

eg: CALCULATOR

- Glowing of LEDs results in displaying numbers
- 0-9 numeric values can be shown.

decimal values	INPUTS				OUTPUTS						
	A	B	C	D	a	b	c	d	e	f	g
0 =	0	0	0	0	→ 1	1	1	1	1	1	0
1 =	0	0	0	1	→ 0	1	1	0	0	0	0
2 =	0	0	1	0	→ 1	1	0	1	1	0	1
3 =	0	0	1	1	→ 1	1	1	1	0	0	1
4 =	0	1	0	0	→ 0	1	1	0	0	1	1
5 =	0	1	0	1	→ 1	0	1	1	0	1	1
6 =	0	1	1	0	→ 1	0	1	1	1	1	1
7 =	0	1	1	1	→ 1	1	1	0	0	0	0
8 =	1	0	0	0	→ 1	1	1	1	1	1	1
9 =	1	0	0	1	→ 1	1	1	1	0	1	1

- 1 represents that LED is ON.
- 0 represents that LED is OFF.

* K-Map for $a =$:

		cd	ab	00	01	11	10
		ab	00	1	0	1	1
		ab	01	0	1	1	1
		ab	11	*	*	*	*
		ab	10	1	1	*	*

$$\begin{aligned} \Rightarrow & \bar{b}\bar{d} + b\bar{d} + \bar{a} + c \\ \Rightarrow & a + c + b \oplus d \end{aligned}$$

* K-Map for $b =$:

		cd	ab	00	01	11	10
		ab	00	1	1	0	1
		ab	01	1	1	1	1
		ab	11	*	*	*	*
		ab	10	1	1	*	*

$$\begin{aligned} \Rightarrow & \bar{b} + \bar{c}\bar{d} + cd \\ \Rightarrow & \bar{b} + c \oplus d \end{aligned}$$

* K-Map for $c =$:

ab	cd	00	01	11	10
00	1	1	1	0	
01	1	1	1	1	
11	*	*	*	*	
10	1	1	*	*	

• $x = b + \bar{c} + cd$

* K-Map for $d =$:

ab	cd	00	01	11	10
00	1	0	1	1	
01	0	1	0	1	
11	*	*	*	*	
10	1	1	*	*	

• $x = \bar{c}\bar{d} + a + b\bar{c}d + c\bar{d} + \bar{a}bc$

* K-Map for $e =$:

ab	cd	00	01	11	10
00	1	0	0	1	
01	0	0	0	1	
11	*	*	*	*	
10	1	0	*	*	

• $x = \bar{c}\bar{d} + cd$

* K-Map for $f =$:

ab	cd	00	01	11	10
00	1	0	0	0	
01	1	1	0	1	
11	*	*	*	*	
10	1	1	*	*	

• $x = \bar{c}\bar{d} + \bar{a}\bar{c} + \bar{a}\bar{d} + a$


* K-Map for $g =$:

ab	cd	00	01	11	10
00	0	0	1	1	
01	1	1	0	1	
11	*	*	*	*	
10	1	1	*	*	

• $x = \bar{c}\bar{a} + a + cd + \bar{b}c$

FLIP - FLOPS

** SR Flip - Flop :

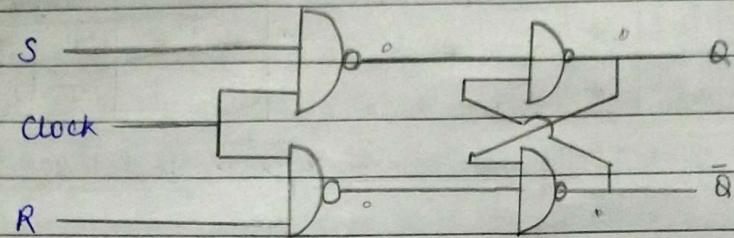

Clock	S	R	Q	\bar{Q}
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	Forbidden Condition	

* CHARACTERISTIC TABLE :

<u>Q</u> (Previous state)	<u>S</u>	<u>R</u>	<u>Q</u> (next state) Output
0	0	0	0
1	0	0	1
0	0	1	0
1	0	1	0
0	1	0	1
1	1	0	1
0	1	1	X
1	1	1	X

(FORBIDDEN CASE)

* EXCITATION TABLE :

Q_1 Previous state Q_2 next state

inputs

0	0
0	1
1	0
1	1

S R
outputs

0	*
1	0
0	1
*	0

value of SR in Ch. Table.


* K-Map:

① For Q_1 :

		00	01	11	10
		0	1		
		1	1	*	*

$$x = q + \bar{s}r$$

** JK Flip-Flop:

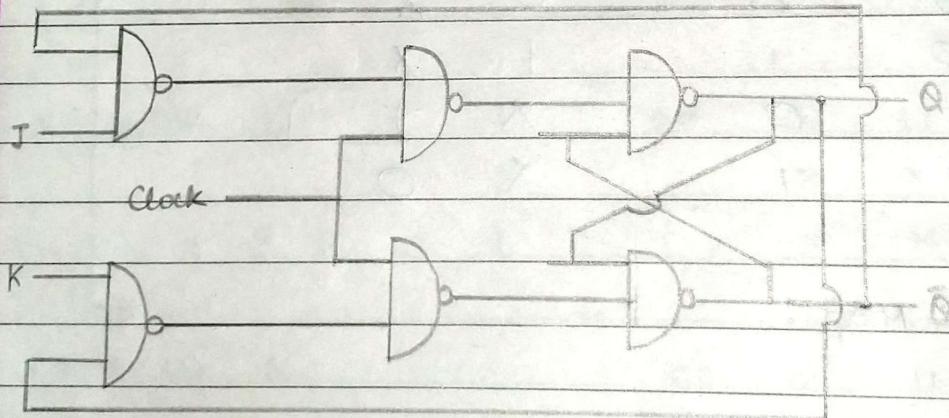

clock J K Q \bar{Q}

1 0 0 Q \bar{Q}

1 0 1 Q 1

1 1 0 1 0

1 1 1 \bar{Q} Q

(Race Round Condition)

* CHARACTERISTIC TABLE :

\bar{Q}_n	J	K	\bar{Q}_n
0	0	0	0
1	0	0	1
0	0	1	0
1	0	1	0
0	1	0	1
1	1	0	1
0	1	1	1
1	1	1	0

* Excitation Table

Input	Output
\bar{Q}_n	J K
0	0 X
0	1 X
1	X 1
1	X 0

* K-Map :

① for Q_n :

* CONVERSION of flipflops:

- JK flipflop to SR flipflops:

↓ ↓

Excitation Characteristic Table
Table.

Characteristic Table:

SR	S	R	Q _n
0 0	0	0	0
0 0	1	1	1
0 1	0	0	0
0 1	1	0	X
1 0	0	1	X
1 0	1	1	1
1 1	0	X	X
1 1	1	X	X

Excitation Table

J	K
0	X
X	0
0	X
X	1
1	X
X	0
X	X
X	X

KMAP for J:

		RQ			
		00	01	11	10
S		0	X	X	
2	S	1	1	X	X

KMAP for K:

		RQ			
		00	01	11	10
S		0			
1					

- SR flipflop to JK Flip flop:

↓ ↓

Characteristic Table

J	K	Q	Q _n
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Excitation Table

S	R
0	*
*	0
0	*
0	1
1	0
*	0
1	0
0	1

- KMAP for R :

J	00	01	11	10
Q	*			
Q _n	1	.	.	1

- KMAP for S :

J	00	01	11	10
Q	*			
Q _n	1	1	*	1

* according to Q_n we can get S R .

* COMPUTER PERFORMANCE *

- * Execution time : formula for performance.

Computer x : 10 s

Computer y : 15 s

- * Relative performance : $\frac{\text{Performance of } x}{\text{Performance of } y} \times \frac{\text{Execution (x)}}{\text{Execution (y)}}$

$$\Rightarrow \frac{\text{execution time (y)}}{\text{execution time (x)}}$$

$$\Rightarrow \frac{15}{10} \rightarrow 1.5 \text{ times faster than y.}$$

- * CPU time :

no. of instructions to be executed \times clock cycle \times no. of seconds.

- clock cycle also known as clock period / clock rate.

ex: ① instructions = 10

clock cycles = 2 (per instruction)

seconds (time) = 30 ns.

$$\Rightarrow 10 \times 2 \times 30 \Rightarrow \underline{600 \text{ ns}}$$

is CPU time.

ex: ② instructions = 1000

↓

, 10 ns.

50% \Rightarrow 3 clock cycles $\Rightarrow (500 \times 3 \times 10)$

20% \Rightarrow 2 clock cycles $\Rightarrow (200 \times 2 \times 10)$

30% \Rightarrow 5 clock cycles $\Rightarrow (300 \times 5 \times 10)$

$$\Rightarrow (500 \times 3 \times 10) + (200 \times 2 \times 10) + (300 \times 5 \times 10)$$

$$\Rightarrow 15000 + 4000 + 15000 \Rightarrow \underline{34000}$$

- clock rate = $\frac{1}{\text{clock period}}$

ns converted to second

$$\Rightarrow 10 \text{ ns} \Rightarrow \frac{1}{10 \times 10^{-9}} \text{ s} = 10^8 \text{ Hz}$$

ex. clock period from clock rate:

$$\text{rate} \Rightarrow 20 \text{ Hz} \Rightarrow 10^{30}$$

$$\Rightarrow \frac{1}{2 \times 10^{30}} \Rightarrow \frac{1}{2} \times 10^{-30} \Rightarrow .5 \times 10^{-30} \text{ seconds.}$$

- AMODHAL'S LAW:

Q: suppose that a task makes extensive use of floating point operations with 40% of the time consumed by floating point operation with a new hardware design. If the floating point module is speed up by factor 4 then what is the overall speedup.

$$\frac{1}{(1-P) + \frac{P}{n}} \longrightarrow \text{parallel fraction}$$

↓ ↓

factor

sequential
factor fraction

(FORMULA for)
AMODHAL'S
LAW

(P) \Rightarrow how much improved

3) $(P) \Rightarrow 40\% \times 0.4 \left(\frac{40}{100} \right)$
 $n = 4$

$\Rightarrow \frac{1}{(1-0.4)} + \frac{0.4}{4} \Rightarrow \frac{1}{0.6+0.1} \Rightarrow \frac{1}{0.7}$ total speedup.

Q: 2) $\frac{1}{(1-P) + \frac{P}{N}} \Rightarrow \frac{1}{(1-0.3) + \frac{0.3}{20}} \Rightarrow \frac{1}{0.7 + \frac{0.3}{20}}$
 $\Rightarrow \frac{1}{17} \Rightarrow \frac{20}{17} \Rightarrow \underline{\underline{1.17}}$

3) $\frac{1}{(1-P) + \frac{P}{n}} \Rightarrow \frac{1}{(1-0.25) + \frac{0.25}{300}} \Rightarrow \frac{1}{0.75 + \frac{25}{300}}$